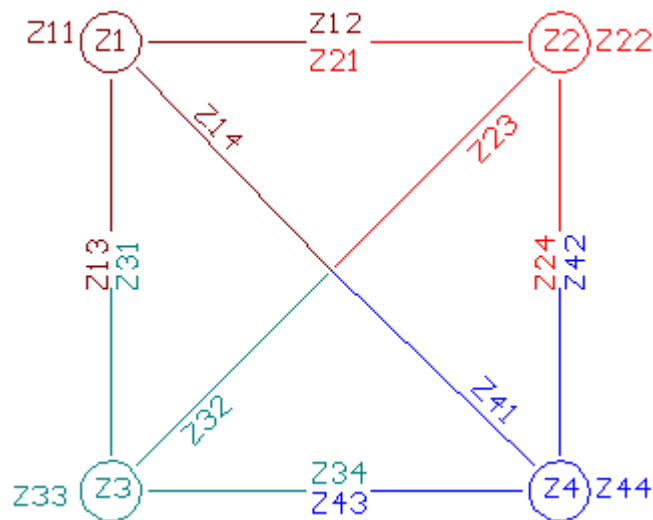


Izračun mutual impedanc 4SQ pri razmaku med elementi $1/4 \lambda$ 

Vnos izmerjenih vrednosti Lastne xx in Medsebojnih (mutual) xy impedanc za vsak element posebej

$$Z_{11} := 21.05 + j \cdot 0.08$$

$$Z_{12} := 19.79 + j \cdot 10.7$$

$$Z_{22} := 21.05 + j \cdot 0.1$$

$$Z_{21} := 19.78 + j \cdot 10.72$$

$$Z_{14} := 26.88 + j \cdot 4.466$$

$$Z_{23} := 26.86 + j \cdot 4.513$$

$$Z_{13} := 19.79 + j \cdot 10.7$$

$$Z_{24} := 19.8 + j \cdot 10.72$$

$$Z_{31} := 19.78 + j \cdot 10.72$$

$$Z_{42} := 19.79 + j \cdot 10.74$$

$$Z_{32} := 26.87 + j \cdot 4.408$$

$$Z_{41} := 26.87 + j \cdot 4.513$$

$$Z_{33} := 21.05 + j \cdot 0.1041$$

$$Z_{34} := 19.79 + j \cdot 10.72$$

$$Z_{44} := 21.06 + j \cdot 0.1212$$

$$Z_{43} := 19.79 + j \cdot 10.73$$

Izračun medsebojnih Impedanc Elementa X proti Elementu Y

$$Z_{m21} := \sqrt{Z_{11} \cdot (Z_{22} - Z_{21})}$$

$$Z_{m12} := \sqrt{Z_{22} \cdot (Z_{11} - Z_{12})}$$

$$Z_{m23} := \sqrt{Z_{33} \cdot (Z_{22} - Z_{23})}$$

$$Z_{m13} := \sqrt{Z_{33} \cdot (Z_{11} - Z_{13})}$$

$$Z_{m24} := \sqrt{Z_{44} \cdot (Z_{22} - Z_{24})}$$

$$Z_{m14} := \sqrt{Z_{44} \cdot (Z_{11} - Z_{14})}$$

$$Z_{m31} := \sqrt{Z_{11} \cdot (Z_{33} - Z_{31})}$$

$$Z_{m41} := \sqrt{Z_{11} \cdot (Z_{44} - Z_{41})}$$

$$Z_{m32} := \sqrt{Z_{22} \cdot (Z_{33} - Z_{32})}$$

$$Z_{m42} := \sqrt{Z_{22} \cdot (Z_{44} - Z_{42})}$$

$$Z_{m34} := \sqrt{Z_{44} \cdot (Z_{33} - Z_{34})}$$

$$Z_{m43} := \sqrt{Z_{33} \cdot (Z_{44} - Z_{43})}$$

Izračunane vrednosti Medsebojnih impedanc.

$$Z_{m12} = 11.241 - 9.938j$$

$$Z_{m21} = 11.241 - 9.939j$$

$$Z_{m13} = 11.242 - 9.937j$$

$$Z_{m23} = 3.984 - 11.735j$$

$$Z_{m14} = 3.962 - 11.745j$$

$$Z_{m24} = 11.243 - 9.94j$$

$$Z_{m31} = 11.239 - 9.937j$$

$$Z_{m41} = 3.96 - 11.732j$$

Stranica

$$Z_{m34} = 11.246 - 9.933j$$

$$Z_{m42} = 11.245 - 9.933j$$

Stranica

$$Z_{m32} = 3.892 - 11.714j$$

$$Z_{m43} = 11.242 - 9.927j$$

Diagonala

Vnos toka in faze za vsak element posebej

$$I1p := 0.9$$

$$I1\theta := -218 \cdot \text{deg}$$

$$I3p := 0.9$$

$$I3\theta := -111 \cdot \text{deg}$$

$$I2p := 0.9$$

$$I2\theta := -111 \cdot \text{deg}$$

$$I4p := 1$$

$$I4\theta := 0 \cdot \text{deg}$$

Pretvorba iz Polar-nega v Kartezični (pravokotni) koordinatni format

$$x1(I1r, I1\theta) := I1r \cdot \cos(I1\theta)$$

$$y1(I1r, I1\theta) := I1r \cdot \sin(I1\theta)$$

$$I1 := x1(I1p, I1\theta) + j \cdot y1(I1p, I1\theta)$$

$$x3(I3p, I3\theta) := I3p \cdot \cos(I3\theta)$$

$$y3(I3p, I3\theta) := I3p \cdot \sin(I3\theta)$$

$$I3 := x3(I3p, I3\theta) + j \cdot y3(I3p, I3\theta)$$

$$I1 = -0.709 + 0.554j$$

$$I3 = -0.323 - 0.84j$$

$$x2(I2p, I2\theta) := I2p \cdot \cos(I2\theta)$$

$$(y2(I2p, I2\theta) := I2p \cdot \sin(I2\theta))$$

$$I2 := x2(I2p, I2\theta) + j \cdot y2(I2p, I2\theta)$$

$$x4(I4p, I4\theta) := I4p \cdot \cos(I4\theta)$$

$$y4(I4p, I4\theta) := I4p \cdot \sin(I4\theta)$$

$$I4 := x4(I4p, I4\theta) + j \cdot y4(I4p, I4\theta)$$

$$I2 = -0.323 - 0.84j$$

$$I4 = 1$$

$$Z1 := Z11 + \frac{I2 \cdot Zm21}{I1} + \frac{I3 \cdot Zm31}{I1} + \frac{I4 \cdot Zm41}{I1}$$

$$Z1 = 21.992 + 34.952j$$

$$Z2 := Z22 + \frac{I1 \cdot Zm12}{I2} + \frac{I3 \cdot Zm32}{I2} + \frac{I4 \cdot Zm42}{I2}$$

$$Z2 = 17.977 - 3.838j$$

$$Z3 := Z33 + \frac{I1 \cdot Zm13}{I3} + \frac{I2 \cdot Zm23}{I3} + \frac{I4 \cdot Zm43}{I3}$$

$$Z3 = 18.065 - 3.862j$$

$$Z4 := Z44 + \frac{I1 \cdot Zm14}{I4} + \frac{I2 \cdot Zm24}{I4} + \frac{I3 \cdot Zm34}{I4}$$

$$Z4 = 0.807 - 1.84j$$

Napetost v točki napajanja elementa

$$VDrive1 := I1 \cdot Z1 \quad VDrive1 = -34.964 - 12.603j$$

$$VDrive2 := I2 \cdot Z2 \quad VDrive2 = -9.023 - 13.867j$$

$$VDrive3 := I3 \cdot Z3 \quad VDrive3 = -9.072 - 13.933j$$

$$VDrive4 := I4 \cdot Z4 \quad VDrive4 = 0.807 - 1.84j$$

$$E1 := (I1 \cdot Z11) + (I2 \cdot Zm12) + (I3 \cdot Zm13) + (I4 \cdot Zm14) \quad E1 = -34.962 - 12.618j$$

$$E2 := (I2 \cdot Z22) + (I1 \cdot Zm21) + (I3 \cdot Zm23) + (I4 \cdot Zm24) \quad E2 = -9.072 - 13.943j$$

$$E3 := (I3 \cdot Z33) + (I1 \cdot Zm31) + (I2 \cdot Zm32) + (I4 \cdot Zm34) \quad E3 = -9.018 - 13.87j$$

$$E4 := (I4 \cdot Z44) + (I1 \cdot Zm41) + (I2 \cdot Zm42) + (I3 \cdot Zm43) \quad E4 = 24.021 - 5.536j$$

Napetost in njeno fazo konvertiramo iz Pravokotne v Polarno vrednost za vsak element posebej.

$$x1 := \text{Re}(VDrive1)$$

$$y1 := \text{Im}(VDrive1)$$

$$r(x1, y1) := \sqrt{x1^2 + y1^2}$$

$$\theta(x1, y1) := \text{angle}(x1, y1)$$

$$\theta(x1, y1) = 199.822 \cdot \text{deg}$$

$$\text{Angle} := \text{if}[(\theta(x1, y1) \leq \pi), (\theta(x1, y1)), \theta(x1, y1) - (2 \cdot \pi)]$$

$$U1 = r(x1, y1) = 37.166$$

V

$$\text{Angle} = -160.178 \cdot \text{deg}$$

$$\begin{aligned} \underline{x2} &:= \text{Re}(\text{VDrive2}) & \underline{y2} &:= \text{Im}(\text{VDrive2}) \\ \underline{r(x2,y2)} &:= \sqrt{x2^2 + y2^2} & \underline{\theta(x2,y2)} &:= \text{angle}(x2,y2) \\ & & \theta(x2,y2) &= 236.948 \cdot \text{deg} \\ \underline{\text{Angle}} &:= \text{if}[(\theta(x2,y2) \leq \pi), (\theta(x2,y2)), \theta(x2,y2) - (2 \cdot \pi)] \\ \underline{U2} &= \underline{r(x2,y2) = 16.544} \quad \underline{V} \quad \underline{\text{Angle} = -123.052 \cdot \text{deg}} \end{aligned}$$

$$\begin{aligned} \underline{x3} &:= \text{Re}(\text{VDrive3}) & \underline{y3} &:= \text{Im}(\text{VDrive3}) \\ \underline{r(x3,y3)} &:= \sqrt{x3^2 + y3^2} & \underline{\theta(x3,y3)} &:= \text{angle}(x3,y3) \\ & & \theta(x3,y3) &= 236.932 \cdot \text{deg} \\ \underline{\text{Angle}} &:= \text{if}[(\theta(x3,y3) \leq \pi), (\theta(x3,y3)), \theta(x3,y3) - (2 \cdot \pi)] \\ \underline{U3} &= \underline{r(x3,y3) = 16.626} \quad \underline{V} \quad \underline{\text{Angle} = -123.068 \cdot \text{deg}} \end{aligned}$$

$$\begin{aligned} \underline{x4} &:= \text{Re}(\text{VDrive4}) & \underline{y4} &:= \text{Im}(\text{VDrive4}) \\ \underline{r(x4,y4)} &:= \sqrt{x4^2 + y4^2} & \underline{\theta(x4,y4)} &:= \text{angle}(x4,y4) \\ & & \theta(x4,y4) &= 293.676 \cdot \text{deg} \\ \underline{\text{Angle}} &:= \text{if}[(\theta(x4,y4) \leq \pi), (\theta(x4,y4)), \theta(x4,y4) - (2 \cdot \pi)] \\ \underline{U4} &= \underline{r(x4,y4) = 2.009} \quad \underline{V} \quad \underline{\text{Angle} = -66.324 \cdot \text{deg}} \end{aligned}$$

$$U4\theta := \text{Angle} \cdot \frac{180}{\pi}$$

$$U4\theta = -66.324$$

V primeru nesimetrije sistema
 zgoraj uporabim vrednosti medsebojnih Impedanc 21, 31, 41
 . Tukaj pa njihove nasprotne vrednosti 12, 13, 14 itd.

$$\begin{aligned} Z1a &:= Z11 + \frac{I2 \cdot Zm12}{I1} + \frac{I3 \cdot Zm13}{I1} + \frac{I4 \cdot Zm14}{I1} & Z2a &:= Z22 + \frac{I1 \cdot Zm21}{I2} + \frac{I3 \cdot Zm23}{I2} + \frac{I4 \cdot Zm24}{I2} \\ Z1a &= 21.98 + 34.964j & Z2a &= 18.076 - 3.859j \end{aligned}$$

$$\begin{aligned} Z3a &:= Z33 + \frac{I1 \cdot Zm31}{I3} + \frac{I2 \cdot Zm32}{I3} + \frac{I4 \cdot Zm34}{I3} & Z4a &:= Z44 + \frac{I1 \cdot Zm41}{I4} + \frac{I2 \cdot Zm42}{I4} + \frac{I3 \cdot Zm43}{I4} \\ Z3a &= 17.978 - 3.832j & Z4a &= 0.813 - 1.853j \end{aligned}$$

$$\text{VDrive1a} := I1 \cdot Z1a \quad \text{VDrive1a} = -34.962 - 12.618j$$

$$\text{VDrive2a} := I2 \cdot Z2a \quad \text{VDrive2a} = -9.072 - 13.943j$$

$$\text{VDrive3a} := I3 \cdot Z3a \quad \text{VDrive3a} = -9.018 - 13.87j$$

$$\text{VDrive4a} := I4 \cdot Z4a \quad \text{VDrive4a} = 0.813 - 1.853j$$

Srednja vrednosti Impedanc Z1 & Z1a; Z2 & Z2a; Z3 & Z3a Z4 & Z4a

$$\begin{aligned} Z1sr &:= \frac{(Z1 + Z1a)}{2} & Z2sr &:= \frac{(Z2 + Z2a)}{2} \\ Z1sr &= 21.986 + 34.958j & Z2sr &= 18.027 - 3.848j \end{aligned}$$

$$\begin{aligned} Z3sr &:= \frac{(Z3 + Z3a)}{2} & Z4sr &:= \frac{(Z4 + Z4a)}{2} \\ Z3sr &= 18.022 - 3.847j & Z4sr &= 0.81 - 1.847j \end{aligned}$$

Srednje vrednosti napetosti v točki napajalnega elementa.

$$V1sr := I1 \cdot Z1sr \quad V1sr = -34.963 - 12.61j$$

$$V2sr := I2 \cdot Z2sr \quad V2sr = -9.048 - 13.905j$$

$$V3sr := I3 \cdot Z3sr \quad V3sr = -9.045 - 13.901j$$

$$V4sr := I4 \cdot Z4sr \quad V4sr = 0.81 - 1.847j$$

Srednje vrednosti napetosti in njenih faz iz Pravokotnega v Polarni format

$$x1 := \text{Re}(V1sr)$$

$$y1 := \text{Im}(V1sr)$$

$$r(x1, y1) := \sqrt{x1^2 + y1^2}$$

$$\theta(x1, y1) := \text{angle}(x1, y1)$$

$$\theta(x1, y1) = 199.833 \cdot \text{deg}$$

$$\text{Angle} := \text{if}[(\theta(x1, y1) \leq \pi), (\theta(x1, y1)), \theta(x1, y1) - (2 \cdot \pi)]$$

$$U1sr = r(x1, y1) = 37.167 \quad V \quad \text{Angle} = -160.167 \cdot \text{deg}$$

$$x2 := \text{Re}(V2sr)$$

$$y2 := \text{Im}(V2sr)$$

$$r(x2, y2) := \sqrt{x2^2 + y2^2}$$

$$\theta(x2, y2) := \text{angle}(x2, y2)$$

$$\theta(x2, y2) = 236.949 \cdot \text{deg}$$

$$\text{Angle} := \text{if}[(\theta(x2, y2) \leq \pi), (\theta(x2, y2)), \theta(x2, y2) - (2 \cdot \pi)]$$

$$U2sr = r(x2, y2) = 16.59 \quad V \quad \text{Angle} = -123.051 \cdot \text{deg}$$

$$x3 := \text{Re}(V3sr) \quad y3 := \text{Im}(V3sr)$$

$$r(x3, y3) := \sqrt{x3^2 + y3^2}$$

$$\theta(x3, y3) := \text{angle}(x3, y3)$$

$$\theta(x3, y3) = 236.95 \cdot \text{deg}$$

$$\text{Angle} := \text{if}[(\theta(x3, y3) \leq \pi), (\theta(x3, y3)), \theta(x3, y3) - (2 \cdot \pi)]$$

$$U3sr = r(x3, y3) = 16.585 \quad V \quad \text{Angle} = -123.05 \cdot \text{deg}$$

$$x4 := \text{Re}(V4sr)$$

$$y4 := \text{Im}(V4sr)$$

$$r(x4, y4) := \sqrt{x4^2 + y4^2}$$

$$\theta(x4, y4) := \text{angle}(x4, y4)$$

$$\theta(x4, y4) = 293.679 \cdot \text{deg}$$

$$\text{Angle} := \text{if}[(\theta(x4, y4) \leq \pi), (\theta(x4, y4)), \theta(x4, y4) - (2 \cdot \pi)]$$

$$U4sr = r(x4, y4) = 2.017 \quad V \quad \text{Angle} = -66.321 \cdot \text{deg}$$

$$Z1 = 21.992 + 34.952j$$

$$Z1a = 21.98 + 34.964j$$

$$Z1sr = 21.986 + 34.958j$$

$$Z2 = 17.977 - 3.838j$$

$$Z2a = 18.076 - 3.859j$$

$$Z2sr = 18.027 - 3.848j$$

$$Z3 = 18.065 - 3.862j$$

$$Z3a = 17.978 - 3.832j$$

$$Z3sr = 18.022 - 3.847j$$

$$Z4 = 0.807 - 1.84j$$

$$Z4a = 0.813 - 1.853j$$

$$Z4sr = 0.81 - 1.847j$$